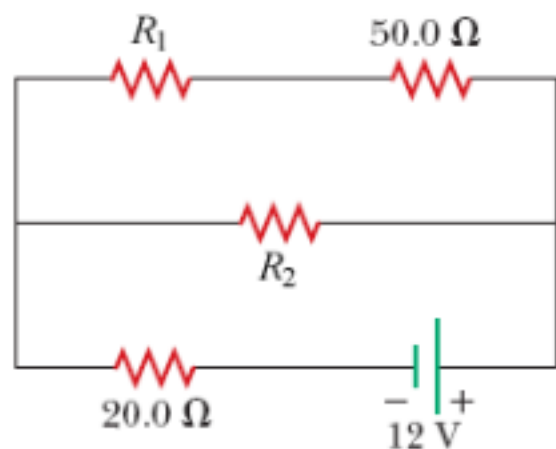


Four resistors are connected to a battery with a terminal voltage of 12 V, as shown in the figure below. (Assume $R_1 = 39.0\ \Omega$ and $R_2 = 89.0\ \Omega$.)



ⓞ

(a) How would you reduce the circuit to an equivalent single resistor connected to the battery? Use this procedure to find the equivalent resistance of the circuit.

Ω

(b) Find the current delivered by the battery to this equivalent resistance.

A

(c) Determine the power delivered by the battery.

W

(d) Determine the power delivered to the 50.0- Ω resistor.

W