Using electricity

Name.....

Look at each circuit below. If you think the bulb will light, colour the bulb yellow and put a tick in the box. If you do not think the bulb will light, put a cross in the box.

