

Name _____ Date _____

Making a Simple Circuit Lab

1. Draw and label a diagram of the circuit you made.

What Did You Learn?

2. How did you make the bulb light? _____

3. What supplied electric current to light the bulb?

Name _____ Date _____

Circuit with a Switch Lab