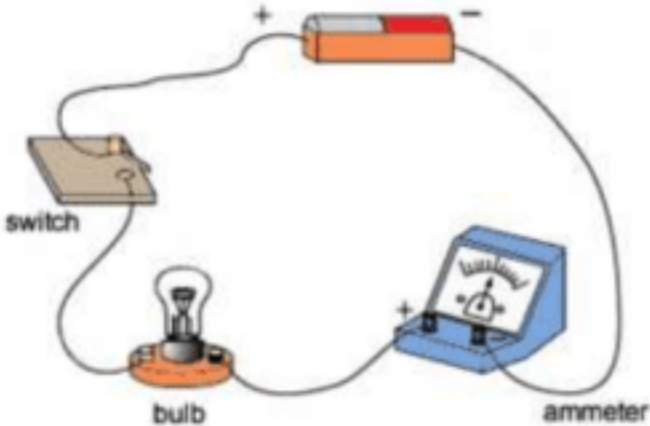
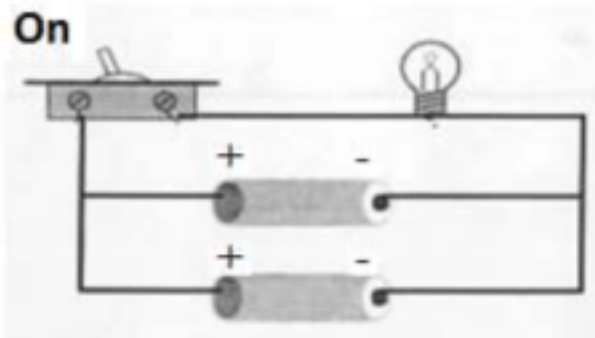
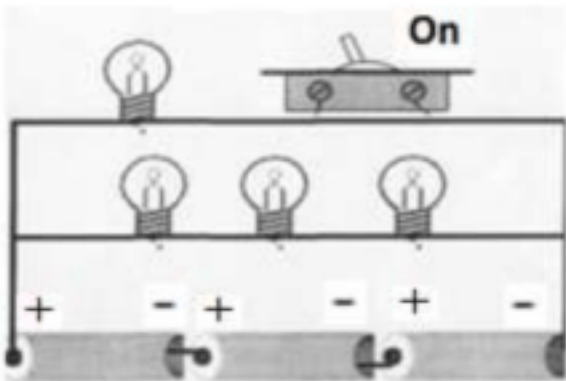


Name: _____

Circuit Diagrams – Practice Worksheet

Instructions: For the following circuits, draw circuit diagrams using circuit symbols. Assume each battery consists of a single cell.

Circuit Picture	Circuit Diagram (Using Circuit Symbols)
<p>#1</p> 	
<p>#2</p> 	
<p>#3</p> 	
<p>#4</p> 