alarm circuit

F 608
BC547
C

BC547

100K

10K

+

3.7V

The led will work when the black wire is cut